

Design Notes Expt 5

Setting the differential input resistance

$$R_{id} = 2r_{be} = \frac{2\beta_o}{g_m} = \frac{2\beta_o}{40I_C}$$

PN2907, value is 254

require $R_{id} > 10k$

So bias current, I_O in differential amplifier is

$$I_O = 2I_C = 2 \frac{2\beta_o}{40R_{id}}$$

$$I_O = \frac{\beta_o}{10R_{id}} = \frac{254}{10 \times 1M} \approx 25 \mu A$$

Now to design the Widlar current mirror to bias the diff amp stage.

$$R_E I_O = V_T \ln\left(\frac{I_{ref}}{I_O}\right) \text{ or } I_{ref} = I_O \exp\left(\frac{I_O R_E}{V_T}\right)$$

Don't know R_E or I_{ref}

? Try $I_O R_E = V_T$

test this & try

Then $I_{ref} = I_O \exp(1)$

*ADP zhishih
OR Set $I_{ref} = 10 \times I_O$ then V_T is thermal vol and is approx 25mV at room temp*

$$R_E = \frac{V_T}{I_O} \ln(10) = \frac{25m}{25\mu} \ln(10) \approx 2.3 k\Omega$$

Resistor in other branch of CM is

$$R = \frac{V_{CC} + V_{EE} - 0.6}{I_{ref}} = \frac{9+9-0.6}{10 \times I_O} = \frac{9+9-0.6}{10 \times 25\mu} = 69.6 k\Omega$$

Gains

Gain of differential amplifier

$$74.03 \quad A_{vd} = \frac{1}{V_T} \frac{V_{An} V_{Ap}}{V_{An} + V_{Ap}} \xrightarrow{PN2907} 115.7 = \frac{1}{25m} \frac{74.03 \times 115.7}{74.03 + 115.7} \approx 1.8 k$$


Gain of CE stage (assume CC gain is unity)

$$A_{VT} \approx A_{vd} \times A_{VCE}$$

$$\text{So } A_{VCE} > \frac{5 \times 10^5}{A_{vd}}$$

$$A_{VCE} = \frac{1}{V_T} \frac{V_{An} V_{Ap}}{V_{An} + V_{Ap}}$$

$$A_{VT} = 1.8k \times 1.8k = 3.2M$$

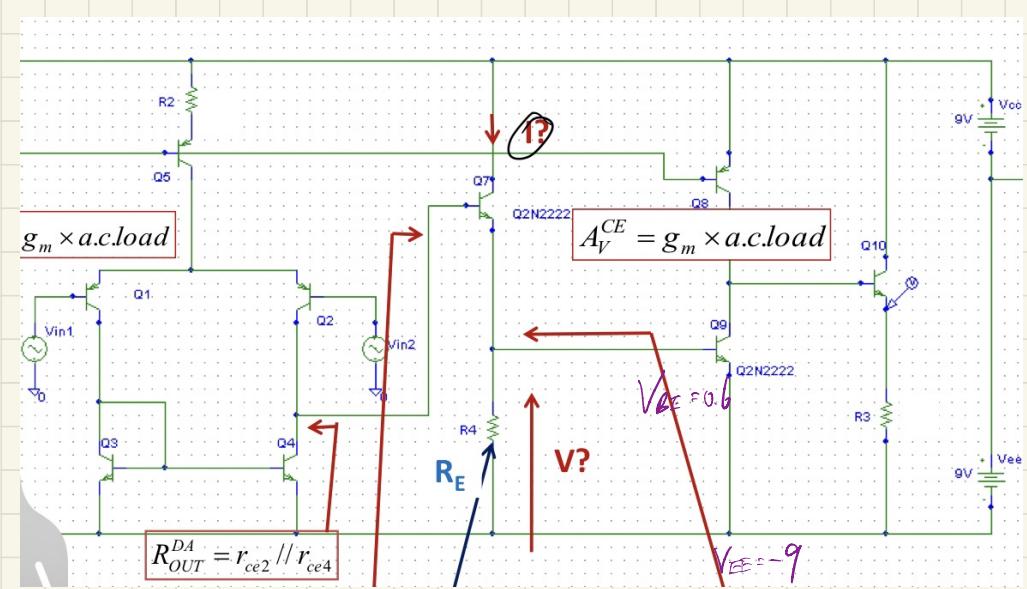

Page 1

$$I_C \approx I_E = \frac{V_{BE}}{R_E}$$

Require $R_i(CC) = 10R_o$

page ②

Sub

$$\frac{\beta_0}{40I_c} + (1+\beta_0) R_E \parallel R_L = 10 \frac{V_{an} V_{ap}}{(V_{an} + V_{ap}) I_c}$$


$$\frac{\beta_0}{40} + I_c (1+\beta_0) R_E \parallel R_L = 10 \frac{V_{an} V_{ap}}{V_{an} + V_{ap}}$$

$$\frac{\beta_0}{40} + I_c (1+\beta_0) \frac{R_E r_{be(CE)}}{R_E + r_{be(CE)}} = 10 \frac{V_{an} V_{ap}}{V_{an} + V_{ap}} \quad \text{--- } ②$$

Sub ① into ②

$$\frac{\beta_0}{40} + \frac{0.6}{R_E} (1+\beta_0) \frac{R_E r_{be(CE)}}{R_E + r_{be(CE)}} = 10 \frac{V_{an} V_{ap}}{V_{an} + V_{ap}}$$
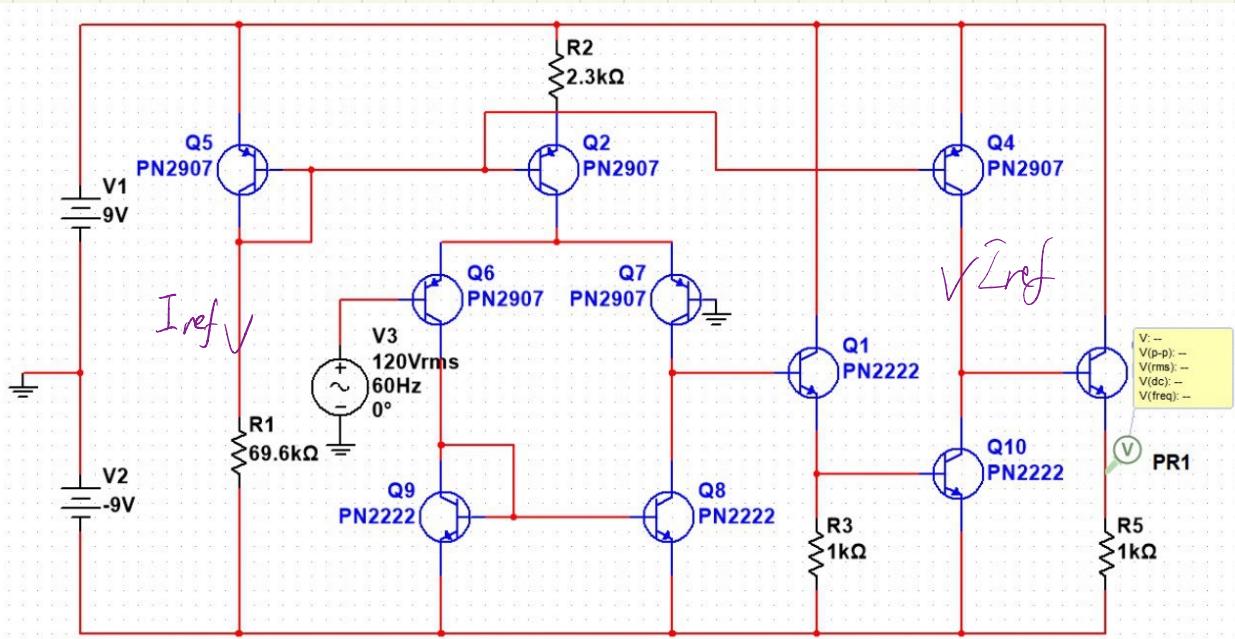
$$\frac{\beta_0}{40} + 0.6 (1+\beta_0) \frac{r_{be(CE)}}{R_E + r_{be(CE)}} = 10 \frac{V_{an} V_{ap}}{V_{an} + V_{ap}} \quad \text{--- } ③$$



$$V_{be}(C_E) = \frac{\beta_0}{4\alpha I_c} = \frac{\beta_0}{4\alpha I_{ref}} \quad \text{---} \quad (4)$$

Sub ④ into ③

$$\frac{\beta_0}{40} + 0.6(1+\beta_0) \frac{\frac{\beta_0}{40I_{ref}}}{R_E + \frac{\beta_0}{40I_{ref}}} = I_0 \frac{V_{An} V_{sp}}{V_{An} + V_{sp}}$$
$$\frac{I_0 \frac{V_{An} V_{sp}}{V_{An} + V_{sp}} - \frac{\beta_0}{40}}{0.6(1+\beta_0)} = \frac{\frac{\beta_0}{40I_{ref}}}{R_E + \frac{\beta_0}{40I_{ref}}}$$

$$R_E = \frac{\beta_0}{40I_{ref}} - \frac{0.6(1+\beta_0)}{I_0 \frac{V_{An} V_{sp}}{V_{An} + V_{sp}} - \frac{\beta_0}{40}} - \frac{\beta_0}{40I_{ref}}$$

$$= \frac{182}{40 \times 250\mu A} - \frac{0.6(1+182)}{I_0 \times \frac{77.03 \times 115.7}{77.03 + 115.7} - \frac{182}{40}} - \frac{182}{40 \times 250\mu A}$$

$$\frac{\beta_o}{g_m} = \frac{\beta_o}{40I_c} \quad ? \quad \text{goto page ①}$$

Calculation for input resistance of CC coupling stage

$$R_i(CC) = r_{be}(CC) + (1 + \beta_o)R_E // R_L$$

$$R_E // R_L = \frac{R_E r_{be}(CE)}{R_E + r_{be}(CE)} \quad \text{PN2222 182}$$

Set $R_i(CC)$ to be much bigger than the output resistance of the Diff/ amp stage (which acts as the source resistance of the CC stage):

$$R_o^{DA} = \frac{\frac{V_{An}}{I_C} \times \frac{V_{Ap}}{I_C}}{\frac{V_{An}}{I_C} + \frac{V_{Ap}}{I_C}} = \frac{V_{An} V_{Ap}}{(V_{An} + V_{Ap}) I_C}$$

(need to try a bias current for the common emitter, CE stage)

Then get a quadratic equation for the CC bias current. Use this to calculate the gain of the CC stage

$$A_V = \frac{g_m R_E // R_L}{1 + g_m R_E // R_L} = \frac{g_m R_E // r_{be}(CE)}{1 + g_m R_E // r_{be}(CE)}$$

Output resistance of op-amp (set by another CC stage)

$$R_o = \frac{r_{be} + R_S}{1 + \beta_o} // R_E, \quad R_o = \left(\frac{r_{be}}{\beta_o} + \frac{R_S}{\beta_o} \right) // R_E \quad \text{This } r_{be} \text{ is that of CC} \quad (\beta_o = g_m r_{be})$$

$$R_o = \left(\frac{r_{be}}{\beta_o} + \frac{R_S}{\beta_o} \right) // \frac{V_{EE}}{I_C}$$

The source resistance, R_S is the output resistance of the previous stage (CE) – see equation for the differential amplifier.


Set R_o to meet the specification; rearranging gives a quadratic equation for this CC bias current.

$$R_o = \left(\frac{\frac{\beta_o}{40I_c}}{\beta_o} + \frac{R_S}{\beta_o} \right) // R_E \quad \frac{1}{R_o} = \frac{1}{R_E} + \frac{R_S}{\beta_o} + \frac{1}{R_E}$$

$$= \left(\frac{1}{40I_c} + \frac{R_S}{\beta_o} \right) // R_E$$

$$= \left(\frac{1}{40R_E} + \frac{R_S}{\beta_o} \right) // R_E$$

$$R_E \approx 111 \Omega$$

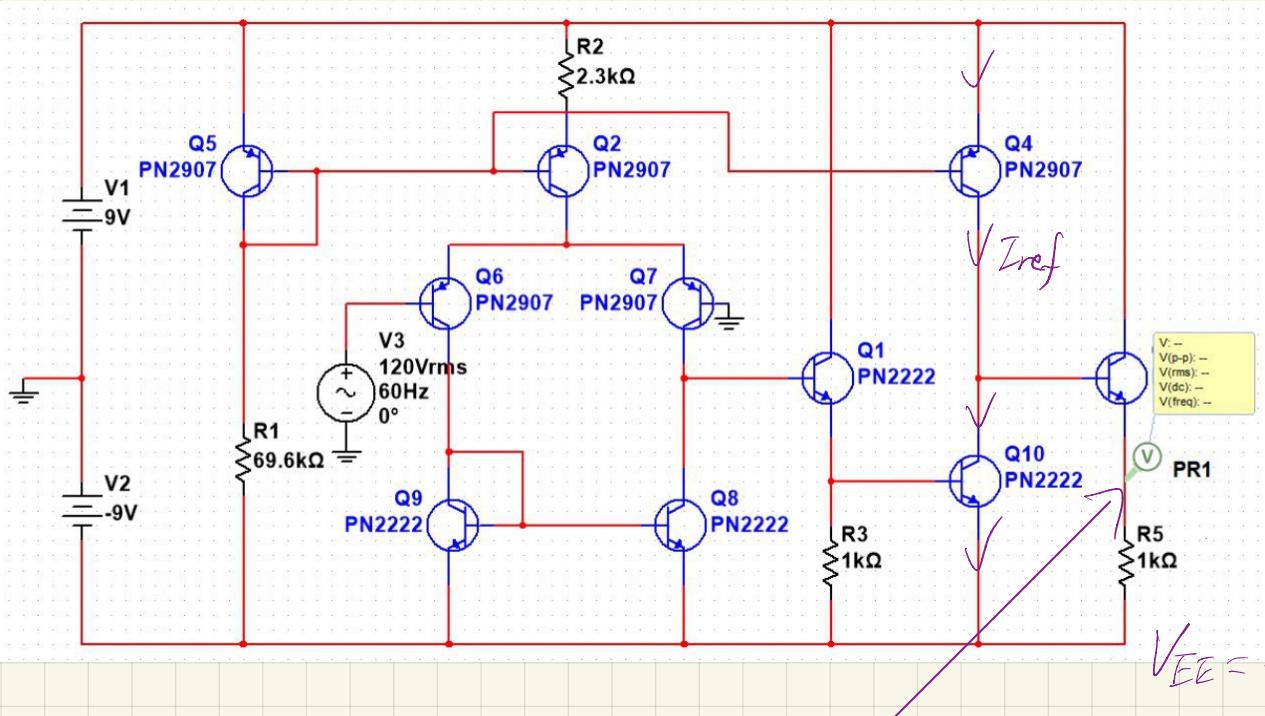

$$V_{EE} = -9V$$

As per specs, DC output vol = 0 V

$$I_C \approx I_E = \frac{0 - (-9)}{R_E}$$

$$= \frac{9}{R_E}$$

$$R_S = r_{CE}^{2907} \parallel r_{CE}^{2222}$$

$$= \frac{V_A^{2907}}{I_{ref}} \parallel \frac{V_A^{2222}}{I_{ref}}$$

$$= \frac{115.7}{250\mu} \parallel \frac{74.03}{250\mu}$$

$$\approx 180k$$